



DIGITAL SYSTEM DESIGN LABORATORY

LAB 6

SINGLE CYCLE MICROPROCESSOR DESIGN

I. LAB OBJECTIVES

This Lab experiments are intended to design and test a Single Cycle Microprocessor

II. DESCRIPTION

Single Cycle Microprocessor datapath to be implemented is in figure 2.1.

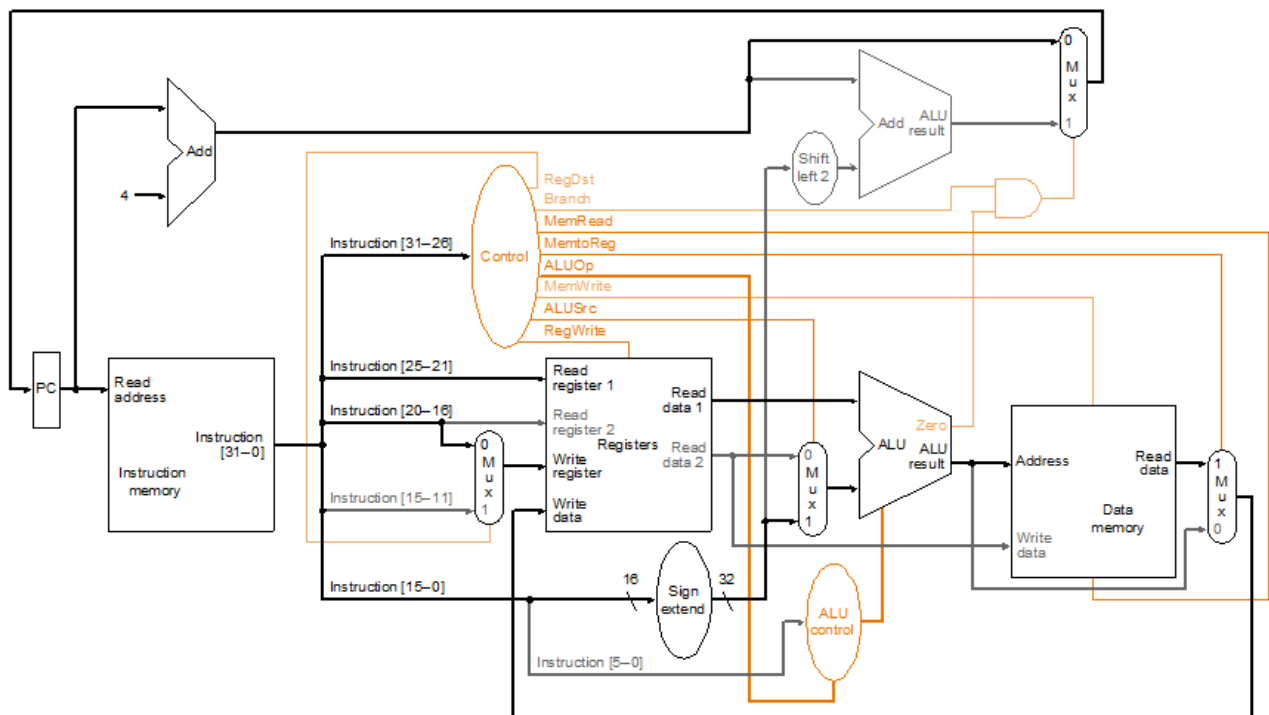


Figure 2.1: Single Cycle Microprocessor DataPath

III. LAB PROCEDURE

III.1 EXPERIMENT NO. 1

III.1.1 AIM: To understand and write the assembly code using MIPS Instruction set

register number of MIPS compiler conventions

Name	Register number	Usage
\$zero	0	the constant value 0
\$v0-\$v1	2-3	values for results and expression evaluation
\$a0-\$a3	4-7	arguments
\$t0-\$t7	8-15	temporaries
\$s0-\$s7	16-23	saved (by callee)
\$t8-\$t9	24-25	more temporaries
\$gp	28	global pointer
\$sp	29	stack pointer
\$fp	30	frame pointer
\$ra	31	return address

MIPS Assembly Language Sumarize:

MIPS assembly language				
Category	Instruction	Example	Meaning	Comments
	add	add \$s1, \$s2, \$s3	\$s1 = \$s2 + \$s3	Three operands; data in registers
Arithmetic	subtract	sub \$s1, \$s2, \$s3	\$s1 = \$s2 - \$s3	Three operands; data in registers
	add immediate	addi \$s1, \$s2, 100	\$s1 = \$s2 + 100	Used to add constants
	load word	lw \$s1, 100(\$s2)	\$s1 = Memory[\$s2 + 100]	Word from memory to register
	store word	sw \$s1, 100(\$s2)	Memory[\$s2 + 100] = \$s1	Word from register to memory
Data transfer	load byte	lb \$s1, 100(\$s2)	\$s1 = Memory[\$s2 + 100]	Byte from memory to register
	store byte	sb \$s1, 100(\$s2)	Memory[\$s2 + 100] = \$s1	Byte from register to memory
	load upper immediate	lui \$s1, 100	\$s1 = 100 * 2 ¹⁶	Loads constant in upper 16 bits
	branch on equal	beq \$s1, \$s2, 25	if (\$s1 == \$s2) go to PC + 4 + 100	Equal test; PC-relative branch
	branch on not equal	bne \$s1, \$s2, 25	if (\$s1 != \$s2) go to PC + 4 + 100	Not equal test; PC-relative
Conditional branch	set on less than	slt \$s1, \$s2, \$s3	if (\$s2 < \$s3) \$s1 = 1; else \$s1 = 0	Compare less than; for beq, bne
	set less than immediate	slti \$s1, \$s2, 100	if (\$s2 < 100) \$s1 = 1; else \$s1 = 0	Compare less than constant
	jump	j 2500	go to 10000	Jump to target address
Uncondi- tional jump	jump register	jr \$ra	go to \$ra	For sw itch, procedure return
	jump and link	jal 2500	\$ra = PC + 4; go to 10000	For procedure call

Operation code (Op code) summarize:


Op	Opcode name	Value
000000	R-format	Rformat1
000010	jmp	JUMP1
000100	beq	BEQ1
100011	lw	Mem1
101011	sw	Mem1

ALU opcode and Function

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)


Instruction Formats

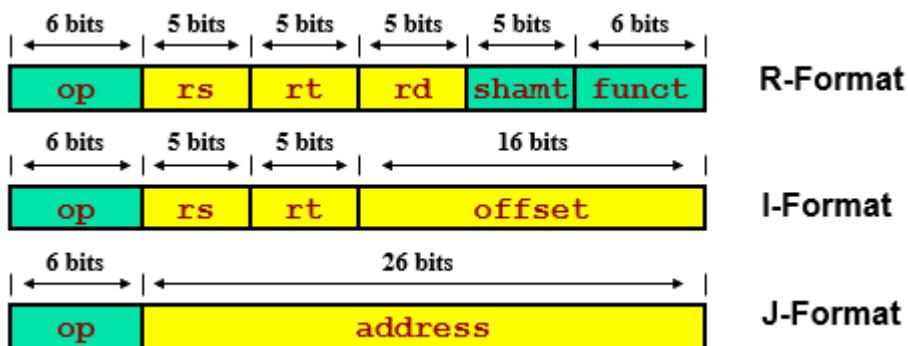

III.1 EXPERIMENT NO. 1

III.1.1 AIM: To implement R-Type Processor

Op	Opcode name	Value
000000	R-format	R-Type
000010	jmp	J-Type
000100	beq	I-Type
100011	lw	
101011	sw	
010000	addi	

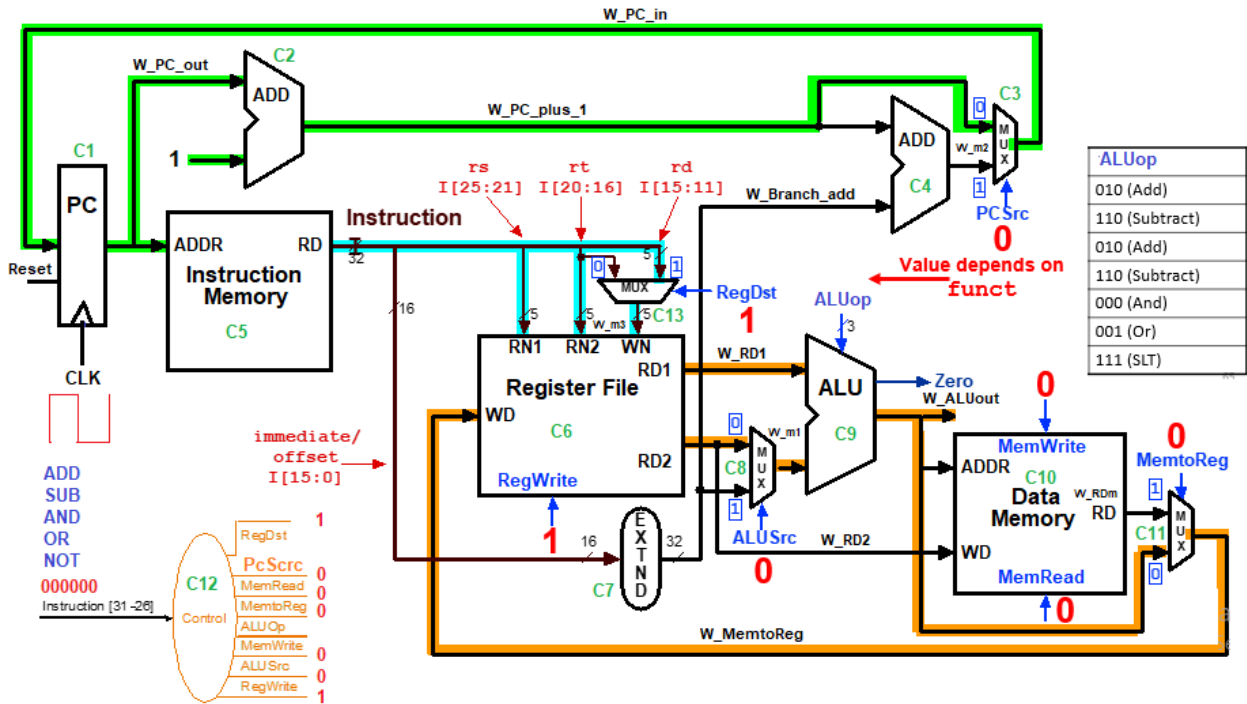

III.1.2 CODE

```

module R_Type_Proc(reset, clk, W_PC_out, instruction, W_RD1,
W_RD2, W_m1, W_m2, W_ALUout);
// Your code here

```

Endmodule

III.1.3 LAB ASSIGNMENT

- 1) Write Verilog code to implement R_Type_Processor module
- 2) Write testbenches to verify R_Type_Processor, simulate and check the simulation output data.
- 3) Write the assembly code with Addition, Substraction instructions, compile into binary machinecode and test the operation of the designed R_Type_Processor processor

```
module lab6_ex1(
    input    CLOCK_50, // PIN_Y2
    input [3:0] KEY,    // KEY[0]: Reset, KEY[1]: Step
    input [17:0] SW,    // SW[1:0]: Chọn dữ liệu hiển thị
    output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, HEX6, HEX7 // 8
    LED 7 đoạn
);

    wire clk_cpu;
    wire reset = !KEY[0]; // KEY0 là Reset (Tích cực thấp)

    // --- BỘ CHỐNG DỘI PHÍM CHO KEY1 (Step) ---
    reg btn_reg1, btn_reg2;
    reg [19:0] debounce_cnt;
    always @(posedge CLOCK_50) begin
        if (debounce_cnt < 20'd1000000)
            debounce_cnt <= debounce_cnt + 1;
        else begin
            debounce_cnt <= 0;
            btn_reg1 <= KEY[1];
            btn_reg2 <= btn_reg1;
        end
    end
    assign clk_cpu = btn_reg2; // Xung nhịp CPU kích bằng nút nhấn

    // --- KẾT NỐI BỘ VI XỬ LÝ (DUT) ---
    wire [31:0] W_PC_out, instruction, W_ALUout, W_MemtoReg;
    wire [31:0] d1, d2, d3, d4;
    wire Jump;

    single_c_Proc CPU (
        .reset(reset),
        .clk(clk_cpu),
        .W_PC_out(W_PC_out), .instruction(instruction),
        .W_RD1(d1), .W_RD2(d2), .W_m1(d3), .W_m2(d4),
        .W_ALUout(W_ALUout), .W_MemtoReg(W_MemtoReg), .Jump(Jump)
    );

    // --- CHỌN DỮ LIỆU 32-BIT ĐỂ HIỂN THỊ ---
    reg [31:0] display_data;
```

```
always @(*) begin
  case(SW[1:0])
    2'b00: display_data = W_PC_out;    // Hiển thị PC 32-bit
    2'b01: display_data = W_ALUout;    // Hiển thị kết quả ALU 32-bit
    2'b10: display_data = W_MemtoReg;  // Hiển thị dữ liệu ghi vào Register
    default: display_data = instruction; // Hiển thị mã máy lệnh hiện tại
  endcase
end

// --- GỌI 8 MODULE HEX7SEG ĐỂ HIỂN THỊ TRỌN VỌNG 32-BIT ---
// Hiển thị từ HEX0 (4-bit thấp nhất) đến HEX7 (4-bit cao nhất)
HEX7SEG h0 (.in(display_data[3:0]), .out(HEX0));
HEX7SEG h1 (.in(display_data[7:4]), .out(HEX1));
HEX7SEG h2 (.in(display_data[11:8]), .out(HEX2));
HEX7SEG h3 (.in(display_data[15:12]), .out(HEX3));
HEX7SEG h4 (.in(display_data[19:16]), .out(HEX4));
HEX7SEG h5 (.in(display_data[23:20]), .out(HEX5));
HEX7SEG h6 (.in(display_data[27:24]), .out(HEX6));
HEX7SEG h7 (.in(display_data[31:28]), .out(HEX7));

endmodule
```