



DIGITAL SYSTEM DESIGN LABORATORY

LAB 1

IMPLEMENTATION OF BASIC COMBINATION LOGIC CIRCUIT USING VERILOG

I. LAB OBJECTIVES

This Lab experiments are intended to implement Basic Combination Logic and Sequential Circuit in Verilog. Students are required to write test bench to simulate the given example code and Top level module to implement these codes in DE2-115 FPGA Kit.

a) For each experiment write the Verilog Code in three methods (dataflow, behavior and gate level)

b) For each model, write the Verilog Code to implement these modules in DE2-FPGA Kit

(Show implementation results in Lab report)

c) For each model, Write the testbench to simulate this module.

(Do this task at home as a Home work 2 and show simulation results in Lab report)

d) Analyze the FPGA implementation results and simulation results for these models

II. PROCEDURE

II.1 LAB EXPERIMENT 1 : WRITE HDL CODE TO REALIZE ALL LOGIC GATES

Refer to the tutorial “Quartus II Introduction Using Verilog Design” to create the first project in Quartus II. implement a simple circuit in DE2-115 Kit.

AND GATE




A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

OR GATE



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

NOT GATE

 

A	\bar{A}
0	1
1	0

NAND GATE



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

NOR GATE



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

XOR GATE



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

XNOR GATE



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1


Top module

```


module Lab1_EX1(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR=SW;
    allgate_DF
DUT(SW[1],SW[0],LEDG[6],LEDG[5],LEDG[4],LEDG[3],LEDG[2],LEDG[1],LEDG[0]);
endmodule

```

Structural	Dataflow	Behavior
<pre> module allgate_GL (a, b, yand,yor,ynot,ynand,ynor,yxor,yx nor); input a,b; output yand, yor, ynot, ynand, ynor, yxor, yxnor; and G1(yand,a,b); or G2(yor,a, b); not G3(ynot,a) ; nand G4 (ynand,a,b); nor G5(ynor,a,b); xor G6(yxor,a,b); xnor G7(yxnor,a,b); endmodule </pre>	<pre> module allgate_DF (a, b, yand,yor,ynot,ynand,ynor,yxor,yx nor); input a,b; output yand, yor, ynot, ynand, ynor, yxor, yxnor; assign yand = a & b; assign yor = a b; assign ynot = ~a ; assign ynand = ~(a & b); assign ynor = ~(a b); assign yxor = a ^ b; assign yxnor =~(a^b); endmodule </pre>	<pre> module allgate_BH (a, b, yand,yor,ynot,ynand,ynor,yxor,yx nor); input a,b; output reg yand, yor, ynot, ynand, ynor, yxor, yxnor always @(*) begin yand <= a & b; yor <= a b; ynot <= ~a ; ynand <= ~(a & b); ynor <= ~(a b); yxor <= a ^ b; yxnor <= ~(a^b); end endmodule </pre>

 

 II.2 LAB EXPERIMENT 2 : WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT THE HALF ADDER CIRCUIT:



Truth Table

A	B	Sum (S)	Carry (Cout)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Top module

```

module Lab1_EX2(SW, LEDG, LEDR);
  input [17:0] SW;
  output [7:0] LEDG;
  output [17:0] LEDR;
  assign LEDR = SW;
  half_adder_DF DUT (
    .a(SW[1]),
    .b(SW[0]),
    .S(LEDG[0]),
    .Cout(LEDG[1])
  );
  assign LEDG[7:2] = 6'b0;
endmodule

```

Structural

```

module half_adder_GL( a, b, S, Cout);
  input a,b;
  output S,Cout;

  xor G1(S,a,b);
  and G2(Cout,a,b);
endmodule

```

Dataflow

```

module half_adder_DF( a, b, S, Cout);
  input a,b;
  output S,Cout;

  assign S = a ^ b;
  assign Cout = a & b;
endmodule

```


Behavior

```


module half_adder_BH( a, b, S, Cout);
  input a,b;
  output reg S,Cout;

  always @(a,b) begin
    S <= a ^ b;
    Cout <= a&b ;
  end
endmodule

```

 

 II.3 EXPERIMENT 3: WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT THE FULL ADDER CIRCUIT:



Inputs			Outputs	
A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Top module

```

module Lab1_EX3(SW, LEDG, LEDR);
    input [17:0] SW;
    output [7:0] LEDG;
    output [17:0] LEDR;

    assign LEDR = SW;


    full_adder_GL FA1(
        .a(SW[0]),
        .b(SW[1]),
        .cin(SW[2]),
        .S(LEDG[0]),
        .Cout(LEDG[1])
    );
endmodule

```




Structural	Dataflow	Behavior using always
<pre>module full_adder_GL(a,b,cin,S,Cout); output S,Cout; input a,b,cin; wire x,y,z; xor g1(x,a,b); xor g2(S,x,cin); and g3(y,x,cin); and g4(z,a,b); or g5(Cout,z,y); endmodule</pre>	<pre>module full_adder_DF(a, b, cin,S, Cout); input a,b,cin; output S, Cout; assign S = a ^ b ^ cin; assign Cout = (a & b) (b & cin) (a & cin); endmodule</pre>	<pre>module full_adder_BH3(a,b,cin,S,Cout); output reg S,Cout; input a,b,cin; always @(a,b,cin) begin S <= a^b^cin; Cout <=(a&b) (b&cin) (cin&a); end endmodule</pre>
Behavior using if else		Behavior using case
<pre>module full_adder_BH2(a, b, cin, S, Cout); input wire a, b, cin; output reg S, Cout; always @(a or b or cin) begin if(a==0 && b==0 && cin==0) begin S=0;Cout=0; end else if(a==0 && b==0 && cin==1) begin S=1;Cout=0; end else if(a==0 && b==1 && cin==0) begin S=1;Cout=0; end else if(a==0 && b==1 && cin==1) begin S=0;Cout=1; end else if(a==1 && b==0 && cin==0) begin S=1;Cout=0; end else if(a==1 && b==0 && cin==1) begin S=0;Cout=1; end else if(a==1 && b==1 && cin==0) begin S=0;Cout=1; end else if(a==1 && b==1 && cin==1)</pre>		<pre>module full_adder_BH1 (a, b, cin, S, Cout); input a,b,cin; output reg S,Cout; always @(a or b or cin) begin case ({a , b , cin}) 3'b000: begin S = 0; Cout = 0; end 3'b001: begin S = 1; Cout = 0; end 3'b010: begin S = 1; Cout = 0; end 3'b011: begin S = 0; Cout = 1; end 3'b100: begin S = 1; Cout = 0; end 3'b101: begin S = 0; Cout = 1; end 3'b110: begin S = 0; Cout = 1; end 3'b111: begin S = 1; Cout = 1; end endcase end endmodule</pre>

 
```
begin
  S=1; Cout=1;
end
end
endmodule
```




II.4 EXPERIMENT 4 : WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT THE RIPPLE CARRY ADDER CIRCUIT:

Ripple Carry Adder-Truth Table

 

A ₁	A ₂	A ₃	A ₄	B ₄	B ₃	B ₂	B ₁	S ₄	S ₃	S ₂	S ₁	Carry
0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	1	0	0	1	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0	1
1	0	1	0	1	0	1	0	0	1	0	0	1
1	1	0	0	1	1	0	0	1	0	0	0	1
1	1	1	0	1	1	1	0	1	1	0	0	1
1	1	1	1	1	1	1	1	1	1	1	0	1

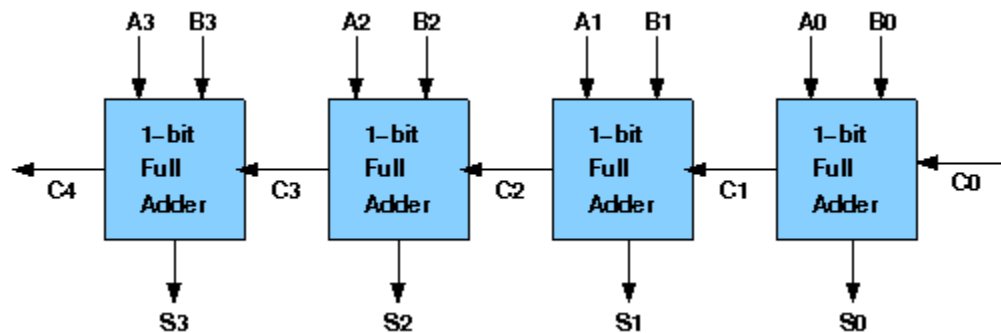



Top module

```
module Lab1_ex4(SW,LEDG,LEDR);
```

```
endmodule
```

Structural

```
module  
full_adder_STRU(a,b,cin,s,cout);  
    output s,cout;  
    input a,b,cin;  
    wire x,y,z;  
    xor g1(x,a,b);  
    xor g2(s,x,cin);  
    and g3(y,x,cin);  
    and g4(z,a,b);  
    or g5(cout,y,z);  
endmodule
```

```
module  
four_bit_adder_STRU(cin,a,b,  
s,cout);  
    input [3:0] a,b;  
    input cin;  
    output [3:0] s;  
    output cout;  
    wire [2:0] w_carry;  
    full_adder_STRU  
C1(a[0],b[0],cin,s[0],  
w_carry[0]);  
    full_adder_STRU  
C2(a[1],b[1], w_carry[0],s[1],  
w_carry[1]);  
    full_adder_STRU  
C3(a[2],b[2], w_carry[1],s[2],  
w_carry[2]);  
    full_adder_STRU  
C4(a[3],b[3], w_carry[2],s[3],  
cout);  
endmodule
```


Dataflow

```
module  
full_adder_DF(a,b,cin,s,cout);  
    input a, b, cin;  
    output Sum, Carry;  
  
    assign Sum = a ^ b ^ cin;  
    assign Carry = (a & b) | (b & cin)  
| (cin & a);  
endmodule  
  
module  
four_bit_adder_DF(a,b,cin,s,cout);  
    input [3:0] a, b;  
    input cin;  
    output [3:0] s;  
    output cout;  
  
    wire [3:0] carry;  
  
    // Assign carry for each bit  
    assign carry[0] = (a[0] & b[0]) |  
(b[0] & cin) | (cin & a[0]);  
    assign carry[1] = (a[1] & b[1]) |  
(b[1] & carry[0]) | (carry[0] &  
a[1]);  
    assign carry[2] = (a[2] & b[2]) |  
(b[2] & carry[1]) | (carry[1] &  
a[2]);  
    assign carry[3] = (a[3] & b[3]) |  
(b[3] & carry[2]) | (carry[2] &  
a[3]);  
  
    // Assign sum for each bit  
    assign s[0] = a[0] ^ b[0] ^ cin;  
    assign s[1] = a[1] ^ b[1] ^  
carry[0];  
    assign s[2] = a[2] ^ b[2] ^  
carry[1];  
    assign s[3] = a[3] ^ b[3] ^  
carry[2];  
endmodule
```


Behavior

```
module half_adder_BH( a, b, s,  
cout);  
    input a,b;  
    output reg s,cout;  
  
    always @(a,b) begin  
        s <= a ^ b;  
        cout <= a&b ;  
    end  
endmodule  
  
module  
four_bit_adder_BH(a,b,cin,s,co  
ut);  
    input [3:0] a, b;  
    input cin;  
    output reg [3:0] s;  
    output reg cout;  
  
    reg [3:0] carry;  
  
    always @(*) begin  
        // Compute sums and  
        carries for each bit using non-  
        blocking assignments  
        s[0] <= a[0] ^ b[0] ^ cin;  
        carry[0] <= (a[0] & b[0]) |  
(b[0] & cin) | (cin & a[0]);  
  
        s[1] <= a[1] ^ b[1] ^  
carry[0];  
        carry[1] <= (a[1] & b[1]) |  
(b[1] & carry[0]) | (carry[0] &  
a[1]);  
  
        s[2] <= a[2] ^ b[2] ^  
carry[1];  
        carry[2] <= (a[2] & b[2]) |  
(b[2] & carry[1]) | (carry[1] &  
a[2]);  
  
        s[3] <= a[3] ^ b[3] ^  
carry[2];  
        cout <= carry[3];  
    end  
endmodule
```


	<pre> assign s[3] = a[3] ^ b[3] ^ carry[2]; // Assign final carry-out assign cout = carry[3]; endmodulex </pre>	<pre> (b[2] & carry[1]) (carry[1] & a[2]); s[3] <= a[3] ^ b[3] ^ carry[2]; cout <= (a[3] & b[3]) (b[3] & carry[2]) (carry[2] & a[3]); end endmodule </pre>
--	--	---

 

 II.5 EXPERIMENT 5 :WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT 2:1 MULTIPLEXER CIRCUIT:



Truth Table

sel	y
0	i_0
1	i_1

Top module

```

module Lab1_EX5(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output [17:0] LEDR;

```

```
assign LEDR=SW;
```

```
//mux21_DF(i(SW[2:1]),.sel(SW[0]),y(LEDG[7]));  
//mux21_BEH(i(SW[2:1]),.sel(SW[0]),y(LEDG[7]));  
mux21_GL(i(SW[2:1]),.sel(SW[0]),y(LEDG[7]));
```

```
endmodule
```

Structural

```
module mux21_GL(i,sel,y);  
    input sel;  
    input [1:0] i;  
    output y;  
    wire net1,net2,net3;  
    not g1(net1,sel);  
    and g2(net2,i[1],sel);  
    and g3(net3,i[0],net1);  
    or g4(y,net3,net2);  
endmodule
```

Dataflow


```
module mux21_DF(i,sel,y);  
    input sel;  
    input [1:0] i;  
    output y;  
    assign y  
    =(i[0]&(~sel))|(i[1]&sel);  
endmodule
```

Behavior


```
module mux21_BEH(i,sel,y);  
    input sel;  
    input [1:0] i;  
    output reg y;  
    always@(*) begin  
        if(sel==0) y=i[0];  
        if(sel==1) y=i[1];  
    end  
endmodule
```



 II.6 EXPERIMENT 6 : WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT 4:1 MULTIPLEXER CIRCUIT:



Block Diagram

 

Truth Table


sel[0]	sel[1]	y
0	0	i ₀
0	1	i ₁
1	0	i ₂
1	1	i ₃

Top module


```
module Lab1_EX6(SW,LEDR,LEDG);
```

```
endmodule
```

Structural	Dataflow	Behavior
<pre>module mux41_GL(i,s,y); input [3:0] i; input [1:0] s; output y; wire [1:0] n_s; wire [3:0] a; not g0(n_s[0],s[0]); not g1(n_s[1],s[1]); and g2(a[0],i[0],n_s[0],n_s[1]); and g3(a[1],i[1],n_s[1],s[0]); and g4(a[2],i[2],s[1],n_s[0]); and g5(a[3],i[3],s[1],s[0]); or g6(y,a[0],a[1],a[2],a[3]); endmodule</pre>	<pre>module mux41_df (i0,i1,i2,i3,s0,s1,y); input i0,i1,i2,i3,s0,s1; output y; assign y= i0&(~s1)&(~s0) i1 &(~s1)&s0 i2&s1&(~s0) i3&s1&s0; endmodule</pre>	<pre>module mux41_BEH_v1(i,s,y); output reg y ; input [3:0] i ; input [1:0] s ; always @ (i,s) begin if (s[1]==0&s[0]==0) y <= i[0]; else if (s[1]==0&s[0]==1) y <= i[1]; else if (s[1]==1&s[0]==0) y <= i[2]; else y <= i[3]; end endmodule Version 2: module mux41_BEH_v2(i,s,y); output reg y ; input [3:0]i; input [1:0]s; always@(i,s) begin case ({s[1],s[0]}) 2'b00: y <= i[0]; 2'b01: y <= i[1]; 2'b10: y <= i[2]; 2'b11: y <= i[3]; endcase end endmodule</pre>

 

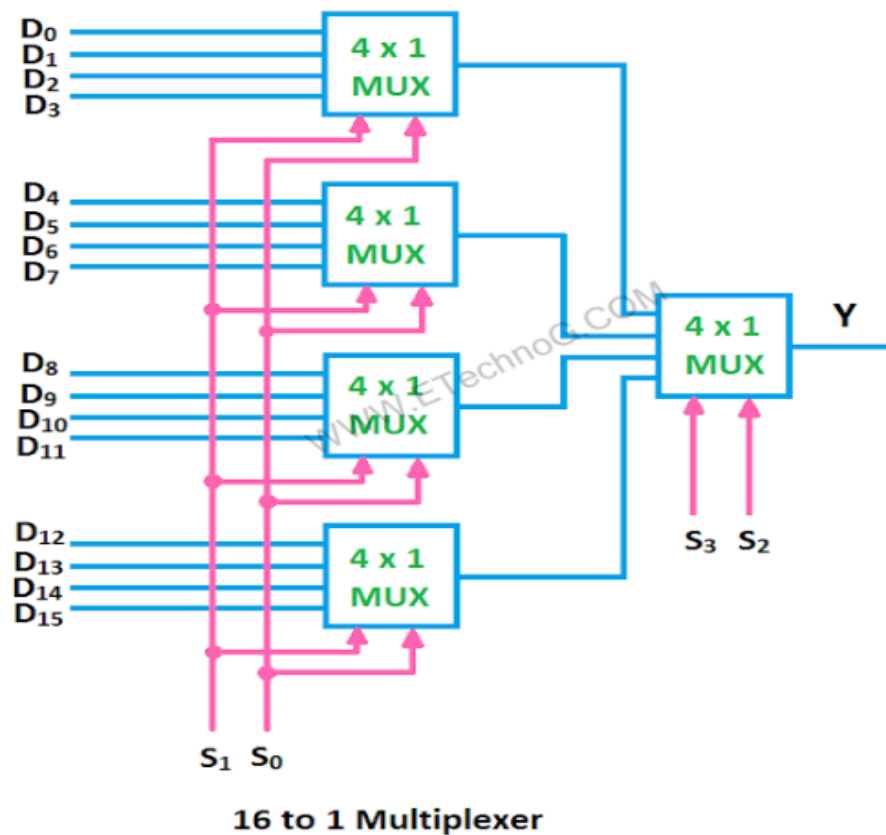II.7 EXPERIMENT 7 : WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT 16:1 MULTIPLEXER CIRCUIT USING STUCTURAL MODEL FROM FIVE 4:1 MULTIPLEXER MODULE



Select				Inputs																Output
S ₃	S ₂	S ₁	S ₀	D ₁₅	D ₁₄	D ₁₃	D ₁₂	D ₁₁	D ₁₀	D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	
0	0	0	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1	1
0	0	0	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1	X	1
0	0	1	0	X	X	X	X	X	X	X	X	X	X	X	X	1	X	X	X	1
0	0	1	1	X	X	X	X	X	X	X	X	X	X	X	1	X	X	X	X	1
0	1	0	0	X	X	X	X	X	X	X	X	X	X	X	1	X	X	X	X	1
0	1	0	1	X	X	X	X	X	X	X	X	X	1	X	X	X	X	X	X	1
0	1	1	0	X	X	X	X	X	X	X	X	1	X	X	X	X	X	X	X	1
0	1	1	1	X	X	X	X	X	X	X	1	X	X	X	X	X	X	X	X	1
1	0	0	0	X	X	X	X	X	X	1	X	X	X	X	X	X	X	X	X	1
1	0	0	1	X	X	X	X	X	1	X	X	X	X	X	X	X	X	X	X	1
1	0	1	0	X	X	X	X	1	X	X	X	X	X	X	X	X	X	X	X	1
1	0	1	1	X	X	X	1	X	X	X	X	X	X	X	X	X	X	X	X	1
1	1	0	0	X	X	1	X	X	X	X	X	X	X	X	X	X	X	X	X	1
1	1	0	1	X	X	1	X	X	X	X	X	X	X	X	X	X	X	X	X	1
1	1	1	0	X	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1
1	1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	1

Answer code:

```

module Lab1_EX7(SW,LEDG,LEDR,KEY);
    input [17:0] SW;
    input [3:0] KEY;
    output [7:0] LEDG;
    output [17:0] LEDR;

    assign LEDR = SW;
    assign LEDG[7:4] = KEY;

    mux16_1(.i0(KEY[3:0]),.i(SW[11:0]),.s(SW[17:14]),.y(LEDG[0]));
endmodule


module mux41_GL(i,s,y);
    input [3:0] i;
    input [1:0] s;
    output y;
    wire n_s0,n_s1, a0,a1,a2,a3;
    not g0(n_s0,s[0]);
    not g1(n_s1,s[1]);
    and g2(a0,i[0],n_s0,n_s1);
    and g3(a1,i[1],n_s1,s[0]);
    and g4(a2,i[2],s[1],n_s0);
    and g5(a3,i[3],s[1],s[0]);
    or g6(y,a0,a1,a2,a3);
endmodule

module mux16_1(i0,i,s,y);
    input [3:0] i0;
    input [11:0] i;
    input [3:0] s;

```


 
```
output y;  
wire [3:0]a;  
  
mux41_GL(i0[3:0],s[1:0],a[0]);  
mux41_GL(i[3:0],s[1:0],a[1]);  
mux41_GL(i[7:4],s[1:0],a[2]);  
mux41_GL(i[11:8],s[1:0],a[3]);  
  
mux41_GL(a[3:0],s[3:2],y)  
endmodule
```





IV. LAB REPORT GUIDELINES

Students write up a report on the Verilog HDL implementation experiment projects created in this lab. The lab report should include Circuit Schematics, Truth Table, Verilog Module Codes, Verilog test bench codes, Top level module to implement the required circuit in FPGA KIT and evidences of data output evidences to validate the experiments (The Captured Screens, Photo of FPGA Kit implementation results).