



DIGITAL SYSTEM DESIGN LABORATORY

LAB 3

IMPLEMENTATION OF ADDERS, SUBTRACTORS, AND MULTIPLIERS USING VERILOG HDL

I. PURPOSE OF THE EXPERIMENT

The purpose of this laboratory exercise is to examine **arithmetic circuits** that add, subtract, and multiply numbers. Each type of circuit shall be implemented in **two ways**: first by writing **Verilog code** that describes the required functionality, and second by making use of **predefined subcircuits** from Altera's library of parameterized modules. The results produced for various implementations will be compared, both in terms of the **circuit structure** and its **speed of operation**. All circuits must be implemented using **pure Verilog structural modeling** with **primitive gates**, **full adders**, and **hierarchical instantiation**.

II. THEORETICAL BACKGROUND

II.1 Ripple-Carry Adder (RCA)

A **ripple-carry adder** is a combinational circuit that performs binary addition by cascading **full adders (FAs)**. For an 8-bit adder:

$$S_i = A_i \oplus B_i \oplus C_i, C_{i+1} = (A_i \cdot B_i) + (A_i \cdot C_i) + (B_i \cdot C_i)$$

- **Carry propagation delay**: The carry signal "ripples" from the least significant bit (LSB) to the most significant bit (MSB).
- **Critical path**: $C_0 \rightarrow C_8$ through 8 full adders.
- **Maximum delay**: $T_{\text{total}} = T_{\text{XOR}} + 8 \times T_{\text{FA}}$
- **Advantage**: Simple, regular structure, easy to model structurally.
- **Disadvantage**: Poor scalability due to $O(n)$ delay.

II.2 Two's Complement Representation and Overflow

In **8-bit two's complement**:

- Range: $[-128, +127]$
- Sign bit: A_7 (0 = positive, 1 = negative)

Overflow occurs when the result of an addition exceeds the representable range:

- Two positive numbers \rightarrow negative result
- Two negative numbers \rightarrow positive result

Overflow detection logic: $\text{Overflow} = (A_7 \cdot B_7 \cdot \neg S_7) + (\neg A_7 \cdot \neg B_7 \cdot S_7)$

This is implemented using **AND**, **NOT**, and **OR** gates.

II.3 Subtraction Using Two's Complement

Subtraction $A - B$ is implemented as: $A - B = A + (\neg B + 1)$

- **Conditional inversion:** $B \oplus \{\text{sub}, \dots, \text{sub}\}$
 - **Carry-in** = sub signal
 - **Unified add/sub circuit** controlled by a single bit.
-

II.4 Binary Multiplication and Array Multiplier

Binary multiplication follows the **shift-and-add** algorithm:

$$P = A \times B = \sum_{i=0}^7 (A \times b_i) \ll i$$

- **Partial products (PPs):** Generated using **AND gates**: $pp_i[j] = a_j \cdot b_i$
 - **Summation:** Performed using **full adders** in a **2D array**
 - **Array multiplier structure:**
 - Regular, scalable, synthesizable
 - Critical path grows diagonally $\rightarrow O(n)$ delay per dimension
-

II.5 Registered Datapath and Pipelining


- **Input registers:** Sample inputs on clock edge \rightarrow eliminate setup/hold violations
 - **Output registers:** Stabilize outputs \rightarrow improve observability
 - **Write Enable (WE):** Controls register loading
 - **Pipelining:** Inserting registers between combinational stages reduces **critical path delay**, increasing **fmax**
-

III. EXPERIMENTAL PROCEDURE

PART I: 8-BIT REGISTERED RIPPLE-CARRY ADDER WITH OVERFLOW

Objective

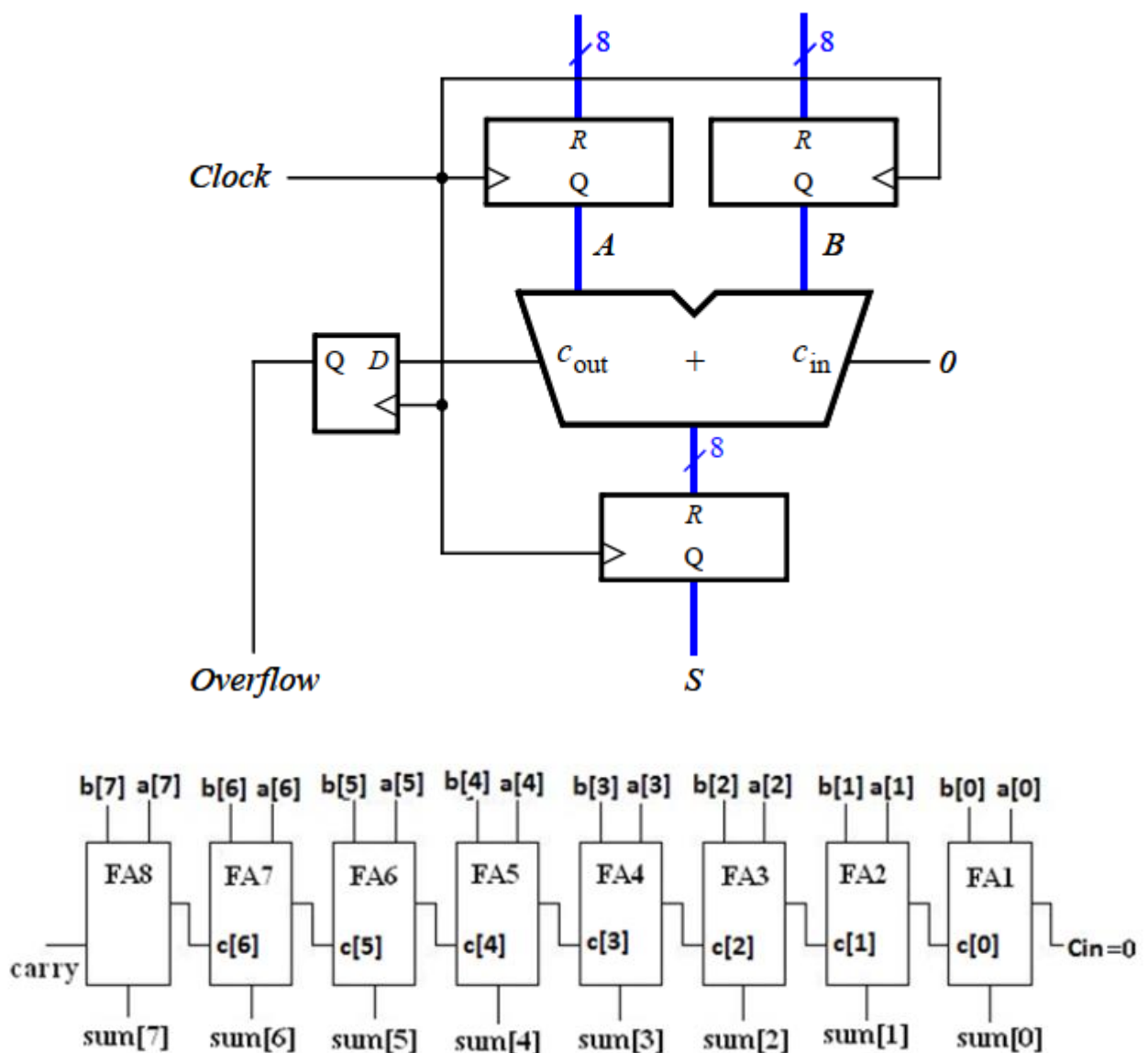Design an 8-bit ripple-carry adder with **registered inputs and outputs**, and **overflow detection** (carry out) using **structural Verilog**.



Step-by-Step Design

1. Gate-Level Full Adder

```
module full_adder (  
    input  wire a, b, cin,  
    output wire sum, cout  
);  
    wire p, g, c1;  
  
    // Propagate and Generate  
    xor (p, a, b);  
    and (g, a, b);  
  
    // Sum  
    xor (sum, p, cin);  
  
    // Carry-out  
    and (c1, p, cin);  
    or  (cout, g, c1);  
endmodule
```

Explanation:

- p = carry propagate
- g = carry generate
- Structural instantiation of primitive gates ensures **no LPM usage**

2. 8-Bit Ripple-Carry Adder (Structural)

```
module eight_bit_adder_stru (  
    input  [7:0] a, b,  
    input        cin,  
    output [7:0] sum,  
    output        cout  
);  
    wire [7:1] carry;
```

```
full_adder fa0 (a[0], b[0], cin,      sum[0], carry[1]);
full_adder fa1 (a[1], b[1], carry[1], sum[1], carry[2]);
full_adder fa2 (a[2], b[2], carry[2], sum[2], carry[3]);
full_adder fa3 (a[3], b[3], carry[3], sum[3], carry[4]);
full_adder fa4 (a[4], b[4], carry[4], sum[4], carry[5]);
full_adder fa5 (a[5], b[5], carry[5], sum[5], carry[6]);
full_adder fa6 (a[6], b[6], carry[6], sum[6], carry[7]);
full_adder fa7 (a[7], b[7], carry[7], sum[7], cout);

endmodule
```

3. Top-Level Module (DE2-115)

```
module lab6_part1 (
    input  [17:0] SW,
    input  [1:0]  KEY,
    output [7:0]  LEDR,
    output [8:0]  LEDG,
    output [6:0]  HEX7, HEX6, HEX5, HEX4, HEX1, HEX0
);

    wire clk = KEY[1], reset_n = KEY[0];
    wire [7:0] A_reg, B_reg, S_reg;
    wire cout, overflow;

    // Input Registers
    dff8 regA (.d(SW[15:8]), .clk(clk), .clrn(reset_n), .q(A_reg));
    dff8 regB (.d(SW[7:0]), .clk(clk), .clrn(reset_n), .q(B_reg));

    // 8-bit Adder
    eight_bit_adder_stru adder (.a(A_reg), .b(B_reg), .cin(1'b0), .sum(S_reg),
    .cout(cout));

    // Output Register
    dff8 regS (.d(S_reg), .clk(clk), .clrn(reset_n), .q(LEDR[7:0]));
```

```
// Overflow Detection

assign overflow = (A_reg[7] & B_reg[7] & ~S_reg[7]) | (~A_reg[7] &
~B_reg[7] & S_reg[7]);

assign LEDG[8] = overflow;


// 7-Segment Displays


hex7seg h7(SW[15:12], HEX7); hex7seg h6(SW[11:8], HEX6);
hex7seg h5(SW[7:4], HEX5); hex7seg h4(SW[3:0], HEX4);
hex7seg h1(LED[7:4], HEX1); hex7seg h0(LED[3:0], HEX0);

endmodule
```

Tasks

1. **Create Quartus Prime project** and write the above Verilog code.
2. **Assign pins:**
 - SW[15:8] → A, SW[7:0] → B
 - KEY[1] → Clock, KEY[0] → Reset
 - LEDR[7:0] → Sum, LEDG[8] → Overflow
3. **Compile and simulate** using ModelSim. Verify overflow cases.
4. **Download to DE2-115** and test with switches.
5. **Open Timing Analyzer** → Report:
 - **fmax**
 - **Longest path delay**
 - **Logic Elements (LEs)**

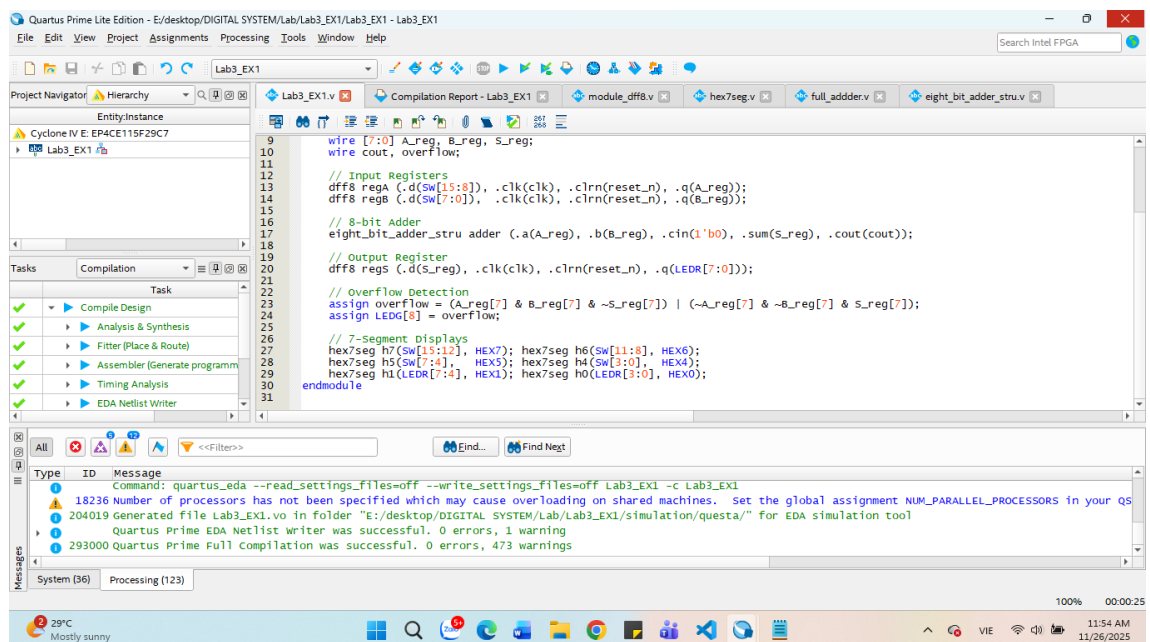


 

PART II: 8-BIT REGISTERED ADDER/SUBTRACTOR

Objective

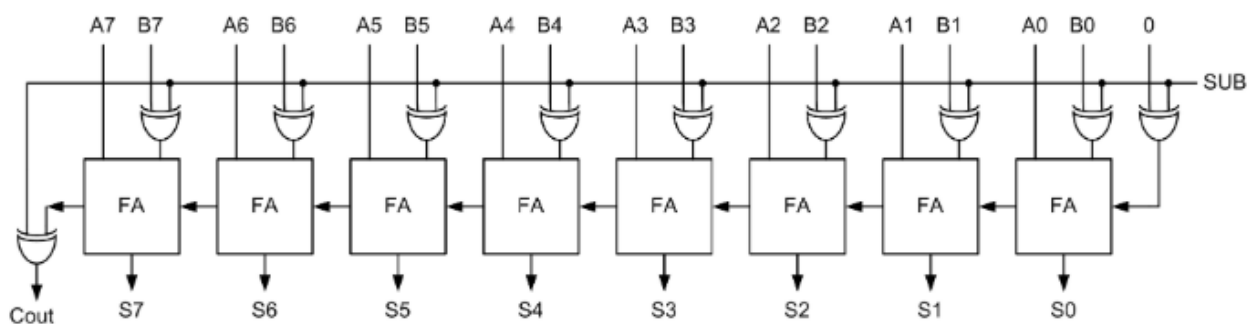Modify Part I to support **addition and subtraction** using a control signal **SUB**.



Theory Recap

- $A - B = A + (\neg B + 1)$
- Use **XOR** to conditionally invert B
- Carry-in = sub

Structural Add/Sub Module

```
module eight_bit_addsub_stru (  
    input  [7:0] a, b,  
    input      sub,  
    output [7:0] sum,  
    output      cout, overflow  
);  
  
    wire [7:0] b_comp;  
    wire [7:1] carry;  
  
    assign b_comp = b ^ {8{sub}}; // Invert B if sub=1  
  
    full_adder fa0 (a[0], b_comp[0], sub, sum[0], carry[1]);  
    full_adder fa1 (a[1], b_comp[1], carry[1], sum[1], carry[2]);  
    full_adder fa2 (a[2], b_comp[2], carry[2], sum[2], carry[3]);  
    full_adder fa3 (a[3], b_comp[3], carry[3], sum[3], carry[4]);  
    full_adder fa4 (a[4], b_comp[4], carry[4], sum[4], carry[5]);  
    full_adder fa5 (a[5], b_comp[5], carry[5], sum[5], carry[6]);  
    full_adder fa6 (a[6], b_comp[6], carry[6], sum[6], carry[7]);  
    full_adder fa7 (a[7], b_comp[7], carry[7], sum[7], cout);  
  
    assign overflow = (a[7] & b_comp[7] & ~sum[7]) | (~a[7] & ~b_comp[7] &  
sum[7]);  
endmodule
```

Top-Level Module

```
module lab6_part2 (  
    input  [17:0] SW,  
    input  [1:0]  KEY,  
    output [7:0]  LEDR,  
    output [8:0]  LEDG,  
    output [6:0]  HEX7, HEX6, HEX5, HEX4, HEX1, HEX0  
);  
  
    wire clk = KEY[1], reset_n = KEY[0], sub = SW[16];  
    wire [7:0] A_reg, B_reg, S_reg;
```

```

wire cout, overflow;

dff8 regA (.d(SW[15:8]), .clk(clk), .clrn(reset_n), .q(A_reg));
dff8 regB (.d(SW[7:0]), .clk(clk), .clrn(reset_n), .q(B_reg));

eight_bit_addsub_stru addsub (.a(A_reg), .b(B_reg), .sub(sub), .sum(S_reg),
.cout(cout), .overflow(overflow));

dff8 regS (.d(S_reg), .clk(clk), .clrn(reset_n), .q(LED7[7:0]));
assign LEDG[8] = overflow;


// 7-segment displays
hex7seg h7(SW[15:12], HEX7); hex7seg h6(SW[11:8], HEX6);
hex7seg h5(SW[7:4], HEX5); hex7seg h4(SW[3:0], HEX4);
hex7seg h1(LED7[7:4], HEX1); hex7seg h0(LED7[3:0], HEX0);


endmodule

```

Tasks

1. Simulate **add** and **subtract** modes.
2. Download to FPGA.
3. Compare **fmax** and **longest path** with Part I.

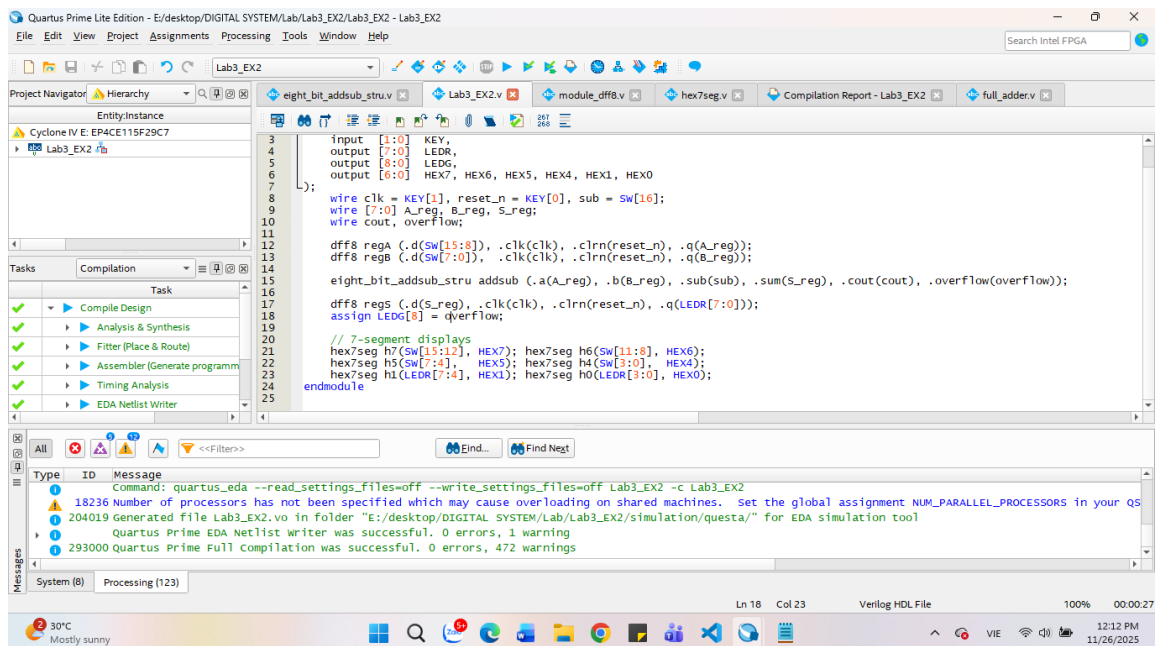


 

PART III: 4-BIT ARRAY MULTIPLIER

Objective

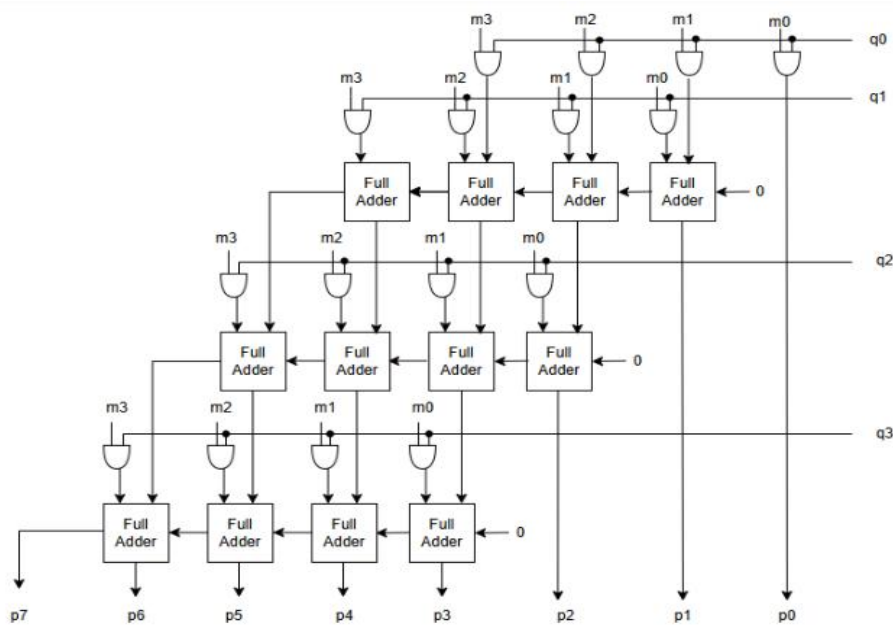Implement a 4×4 array multiplier using AND gates and full adders.



```
module array_multiplier_4x4 (  
    input  [3:0] a, b,  
    output [7:0] p  
);  
  
    wire [3:0] pp0, pp1, pp2, pp3;  
    wire [6:0] c;  
  
    assign pp0 = a & {4{b[0]}};  
    assign pp1 = a & {4{b[1]}};  
    assign pp2 = a & {4{b[2]}};  
    assign pp3 = a & {4{b[3]}};  
  
    assign p[0] = pp0[0];  
    full_adder fa00 (pp0[1], pp1[0], 1'b0, p[1], c[0]);  
  
    full_adder fa10 (pp0[2], pp1[1], c[0], p[2], c[1]);  
    full_adder fa11 (pp0[3], pp1[2], c[1], p[3], c[2]);  
    full_adder fa12 (pp1[3], 1'b0, c[2], p[4], c[3]);  
  
    full_adder fa20 (pp2[1], c[3], 1'b0, p[5], c[4]);  
    full_adder fa21 (pp2[2], c[4], 1'b0, p[6], c[5]);  
    full_adder fa22 (pp2[3], c[5], 1'b0, p[7], c[6]);  
  
    assign p[7] = pp3[3] ^ c[6];  
endmodule
```

Top-Level 4-Bit Multiplier



```
module lab6_part3 (  
    input  [11:0] SW,  
    output [6:0]  HEX6, HEX4, HEX1, HEX0  
);  
  
    wire [7:0] p;  
  
    array_multiplier_4x4 mult (.a(SW[11:8]), .b(SW[3:0]), .p(p));  
  
    hex7seg h6(SW[11:8], HEX6); hex7seg h4(SW[3:0], HEX4);
```

```
hex7seg h1(p[7:4], HEX1);    hex7seg h0(p[3:0], HEX0);

endmodule
```

Tasks


1. Simulate and verify with testbench.
2. Display A, B, Pon 7-segment displays.
3. Test on DE2-115.

 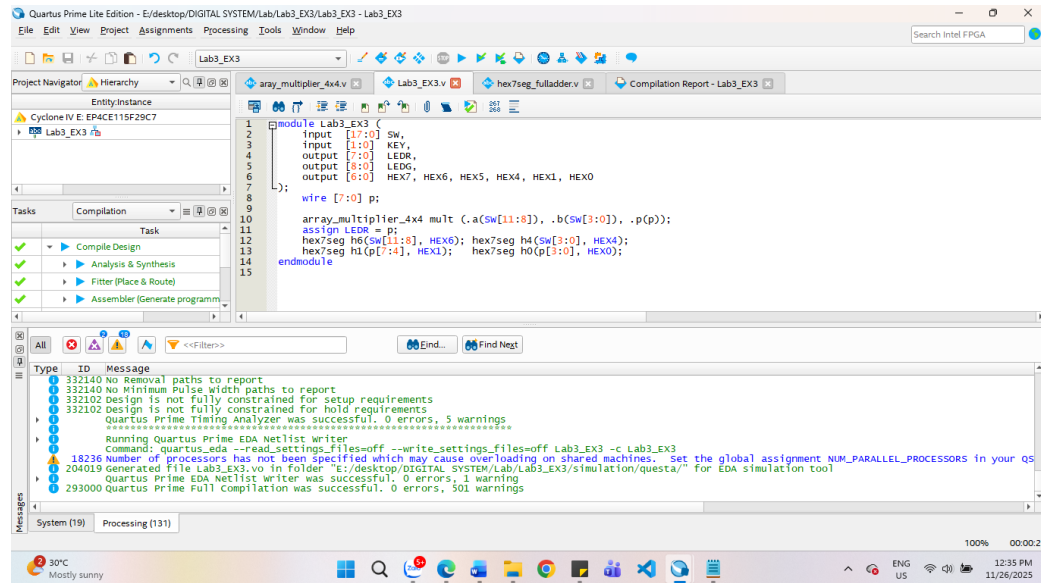

PART IV: 8-BIT REGISTERED ARRAY MULTIPLIER

Objective

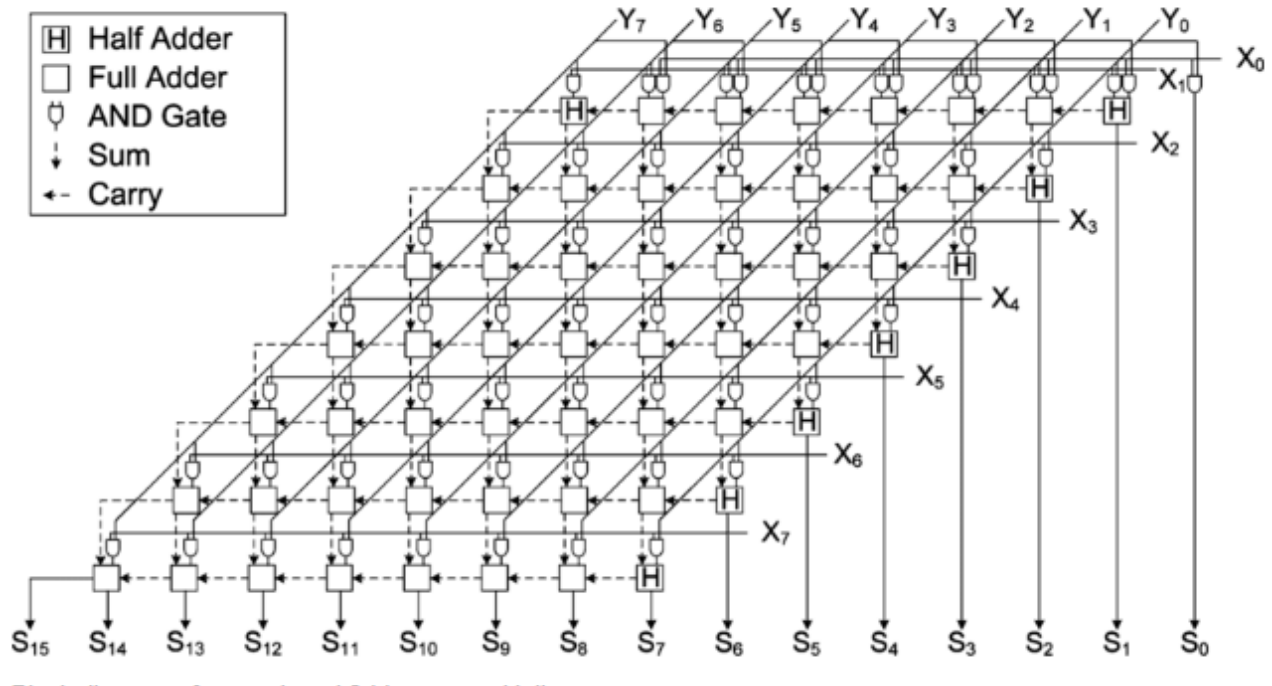Extend the 4-bit multiplier to $8 \times 8 \rightarrow 16$ -bit with input/output registers.



8x8 Array Multiplier (Hierarchical)


```
module array_multiplier_8x8 (
    input  [7:0] a, b,
    input      clk, clrn,
    output [15:0] p
);
    wire [7:0] A_reg, B_reg;
    wire [15:0] p_comb;

    dff8 regA (.d(a), .clk(clk), .clrn(clrn), .q(A_reg));
    dff8 regB (.d(b), .clk(clk), .clrn(clrn), .q(B_reg));

    // Full 8x8 array (use generate or hierarchical 4x4 blocks)
    // ... (complex - implement using generate loops)
```

```
dff16 regP (.d(p_comb), .clk(clk), .clrn(clrn), .q(p));

endmodule
```

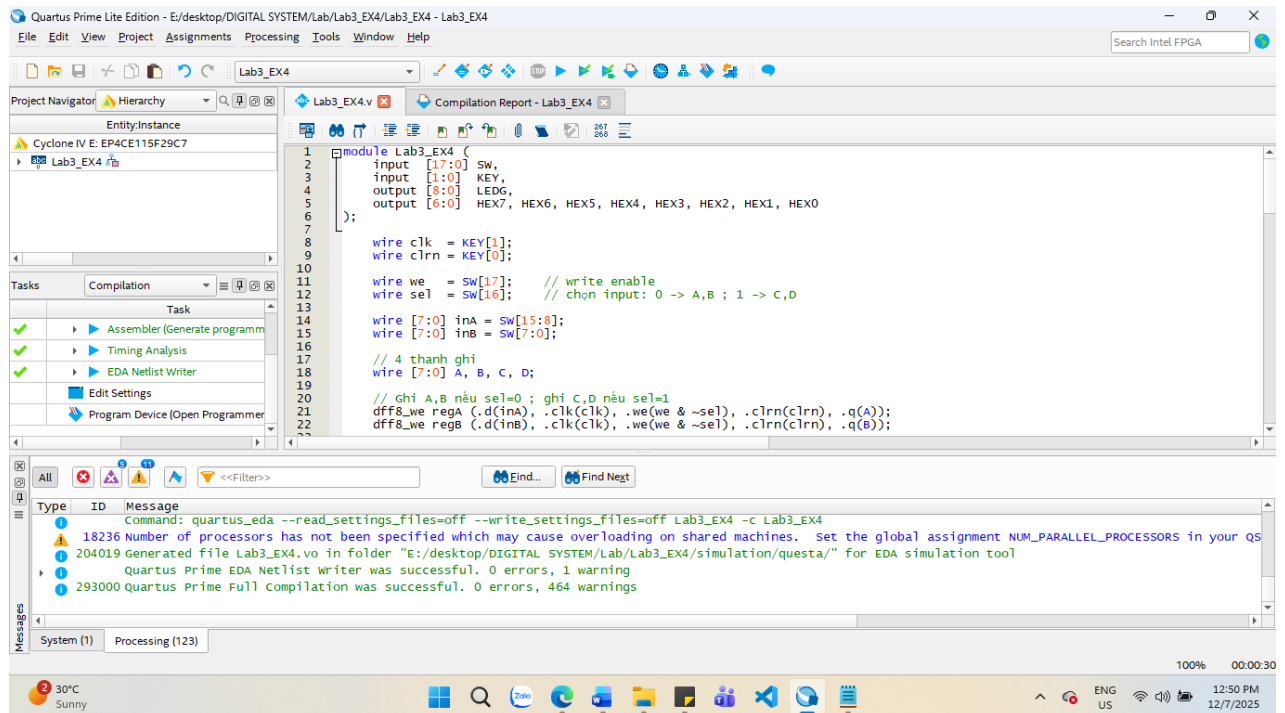

PART V: $S = (A \times B) + (C \times D)$ WITH WRITE ENABLE

Objective

Implement a **registered MAC unit with write enable and input selection.**

Top-Level MAC Unit

```
module lab6_part5 (
    input  [17:0] SW,
    input  [1:0]  KEY,
    output [8:0]  LEDG,
    output [6:0]  HEX7, HEX6, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0
);

    wire clk = KEY[1], clrn = KEY[0], we = SW[17], sel = SW[16];
    wire [7:0] A, B, C, D, inA, inB;
```



```
wire [15:0] P1, P2, Sum;

wire cout;

assign inA = sel ? SW[15:8] : SW[15:8];
assign inB = sel ? SW[7:0] : SW[7:0];

dff8_we regA (.d(inA), .clk(clk), .we(we), .clrn(clrn), .q(A));
dff8_we regB (.d(inB), .clk(clk), .we(we), .clrn(clrn), .q(B));
// Repeat for C, D

array_multiplier_8x8 mult1 (.a(A), .b(B), .clk(clk), .clrn(clrn), .p(P1));
array_multiplier_8x8 mult2 (.a(C), .b(D), .clk(clk), .clrn(clrn), .p(P2));

eight_bit_addsub_stru adder16 (.a(P1), .b(P2), .sub(1'b0), .sum(Sum),
.cout(cout));

dff16 regSum (.d(Sum), .clk(clk), .clrn(clrn), .q({HEX3,HEX2,HEX1,HEX0}));
assign LEDG[8] = cout;
endmodule
```

IV. SUPPORT MODULES

```
module dff8(input [7:0] d, input clk, clrn, output reg [7:0] q);
    always @(posedge clk or negedge clrn)
        if (!clrn) q <= 0; else q <= d;
endmodule

module dff8_we(input [7:0] d, input clk, we, clrn, output reg [7:0] q);
    always @(posedge clk or negedge clrn)
        if (!clrn) q <= 0; else if (we) q <= d;
endmodule

module dff16(input [15:0] d, input clk, clrn, output reg [15:0] q);
    always @(posedge clk or negedge clrn)
        if (!clrn) q <= 0; else q <= d;
endmodule
```




```
module hex7seg(input [3:0] hex, output reg [6:0] seg);  
    always @(*) case(hex)  
        0: seg = 7'b1000000; 1: seg = 7'b1111001;  
        2: seg = 7'b0100100; 3: seg = 7'b0110000;  
        4: seg = 7'b0011001; 5: seg = 7'b0010010;  
        6: seg = 7'b0000010; 7: seg = 7'b1111000;  
        8: seg = 7'b0000000; 9: seg = 7'b0010000;  
        10: seg = 7'b0001000; 11: seg = 7'b0000011;  
        12: seg = 7'b1000110; 13: seg = 7'b0100001;  
        14: seg = 7'b0000110; 15: seg = 7'b0001110;  
    endcase  
endmodule
```

V. LAB REPORT REQUIREMENTS

Section	Content
1. Introduction	Purpose, theory summary
2. Design	Schematics, Verilog code (all parts)
3. Simulation	ModelSim waveforms
4. FPGA Results	Photos, LED/7-seg displays
8. Conclusion	Key findings, challenges

IV. LAB REPORT GUIDELINES

Students write up a report on the Verilog HDL implementation experiment projects created in this lab. The lab report should include Circuit Schematics, Truth Table, Verilog Module Codes, Verilog test bench codes, Top level module to implement the required circuit in FPGA KIT and evidences of data output evidences to validate the experiments (The Captured Screens, Photo of FPGA Kit implementation results).